

20.0°C value, find the length of wire used. (b) **What If?** Now consider the variation of resistivity with temperature. What power is delivered to the coil of part (a) when it is warmed to 1 200°C?

32. Why is the following situation impossible? A politician is decrying wasteful uses of energy and decides to focus on energy used to operate plug-in electric clocks in the United States. While many people use their smartphone as an alarm clock, he estimates that there are still 270 million plug-in alarm clocks in continuous use. The clocks transform energy taken in by electrical transmission at the average rate 2.50 W. The politician gives a speech in which he complains that, at today's electrical rates, the nation is losing \$100 million every year to operate these clocks.
33. Make an order-of-magnitude estimate of the cost of one person's routine use of a handheld hair dryer for 1 year. If you do not use a hair dryer yourself, observe or interview someone who does. State the quantities you estimate and their values.

ADDITIONAL PROBLEMS

34. Lightbulb A is marked "25 W 120 V," and lightbulb B is marked "100 W 120 V." These labels mean that each lightbulb has its respective power delivered to it when it is connected to a constant 120-V source. (a) Find the resistance of each lightbulb. (b) During what time interval does 1.00 C pass into lightbulb A? (c) Is this charge different upon its exit versus its entry into the lightbulb? Explain. (d) In what time interval does 1.00 J pass into lightbulb A? (e) By what mechanisms does this energy enter and exit the lightbulb? Explain. (f) Find the cost of running lightbulb A continuously for 30.0 days, assuming the electric company sells its product at \$0.110 per kWh.
35. One wire in a high-voltage transmission line carries 1 000 A starting at 700 kV for a distance of 100 mi. If the resistance in the wire is 0.500 Ω /mi, what is the power loss due to the resistance of the wire?

36. You are working with an oceanographer who is studying how the ion concentration in seawater depends on depth. She shows you the device that she uses to measure the resistivity of water from a boat. It consists of a pair of concentric metallic cylinders at the end of a cable (Fig. P26.36). Seawater flows freely between the two cylindrical shells. She makes a measurement by lowering the device into the water and applying a potential difference ΔV between the inner and outer cylinders. This produces an outward radial current I in the seawater between the shells. She shows you the current and voltage data for the water at a particular depth and is then called away to answer a long call on her cellphone about a laboratory issue back on the mainland. As she leaves, she says, "Have the resistivity of the water calculated when I get back." She forgot to show you any tables or formulas to use to determine the resistivity, so you are on your own. Quick! Find an expression for the resistivity in terms of I and ΔV before she finishes her phone call!

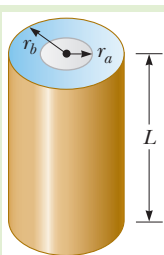


Figure P26.36

37. A charge Q is placed on a capacitor of capacitance C . The capacitor is connected into the circuit shown in Figure P26.37, with an open switch, a resistor, and an initially

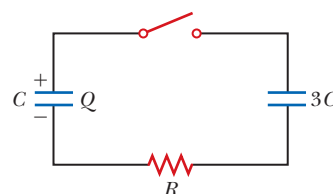


Figure P26.37

uncharged capacitor of capacitance $3C$. The switch is then closed, and the circuit comes to equilibrium. In terms of Q and C , find (a) the final potential difference between the plates of each capacitor, (b) the charge on each capacitor, and (c) the final energy stored in each capacitor. (d) Find the internal energy appearing in the resistor.

38. An experiment is conducted to measure the electrical resistivity of Nichrome in the form of wires with different lengths and cross-sectional areas. For one set of measurements, a student uses 30-gauge wire, which has a cross-sectional area of $7.30 \times 10^{-8} \text{ m}^2$. The student measures the potential difference across the wire and the current in the wire with a voltmeter and an ammeter, respectively. (a) For each set of measurements given in the table taken on wires of three different lengths, calculate the resistance of the wires and the corresponding values of the resistivity. (b) What is the average value of the resistivity? (c) Explain how this value compares with the value given in Table 26.2.

L (m)	ΔV (V)	I (A)	R (Ω)	ρ ($\Omega \cdot \text{m}$)
0.540	5.22	0.72		
1.028	5.82	0.414		
1.543	5.94	0.281		

39. A straight, cylindrical wire lying along the x axis has a length of 0.500 m and a diameter of 0.200 mm. It is made of a material described by Ohm's law with a resistivity of $\rho = 4.00 \times 10^{-8} \Omega \cdot \text{m}$. Assume a potential of 4.00 V is maintained at the left end of the wire at $x = 0$. Also assume $V = 0$ at $x = 0.500$ m. Find (a) the magnitude and direction of the electric field in the wire, (b) the resistance of the wire, (c) the magnitude and direction of the electric current in the wire, and (d) the current density in the wire. (e) Show that $E = \rho J$.
40. A straight, cylindrical wire lying along the x axis has a length L and a diameter d . It is made of a material described by Ohm's law with a resistivity ρ . Assume potential V is maintained at the left end of the wire at $x = 0$. Also assume the potential is zero at $x = L$. In terms of L , d , V , ρ , and physical constants, derive expressions for (a) the magnitude and direction of the electric field in the wire, (b) the resistance of the wire, (c) the magnitude and direction of the electric current in the wire, and (d) the current density in the wire. (e) Show that $E = \rho J$.

41. **Review.** An office worker uses an immersion heater to warm 250 g of water in a light, covered, insulated cup from 20.0°C to 100°C in 4.00 min. The heater is a Nichrome resistance wire connected to a 120-V power supply. Assume the wire is at 100°C throughout the 4.00-min time interval. (a) Specify a relationship between a diameter and a length that the wire can have. (b) Can it be made from less than 0.500 cm³ of Nichrome?

42. The strain in a wire can be monitored and computed by measuring the resistance of the wire. Let L_i represent the original length of the wire, A_i its original cross-sectional area, $R_i = \rho L_i / A_i$ the original resistance between its ends, and $\delta = \Delta L / L_i = (L - L_i) / L_i$ the strain resulting from the application of tension. Assume the resistivity and the volume of the wire do not change as the wire stretches. (a) Show that the resistance between the ends of the wire under strain is given by $R = R_i(1 + 2\delta + \delta^2)$. (b) If the assumptions are precisely true, is this result exact or approximate? Explain your answer.

43. A close analogy exists between the flow of energy by heat because of a temperature difference (see Section 19.6) and the flow of electric charge because of a potential difference. In a metal, energy dQ and electrical charge dq are both transported by free electrons. Consequently, a good electrical conductor is usually a good thermal conductor as well. Consider a thin conducting slab of thickness dx , area A , and electrical conductivity σ , with a potential difference dV between opposite faces. (a) Show that the current $I = dq/dt$ is given by the equation on the left:

Charge conduction	Thermal conduction
$\frac{dq}{dt} = \sigma A \left \frac{dV}{dx} \right $	$\frac{dQ}{dt} = kA \left \frac{dT}{dx} \right $

In the analogous thermal conduction equation on the right (Eq. 19.17), the rate dQ/dt of energy flow by heat (in SI units of joules per second) is due to a temperature gradient dT/dx in a material of thermal conductivity k . (b) State analogous rules relating the direction of the electric current to the change in potential and relating the direction of energy flow to the change in temperature.

44. The dielectric material between the plates of a parallel-plate capacitor always has some nonzero conductivity σ . Let A represent the area of each plate and d the distance between them. Let κ represent the dielectric constant of the material. (a) Show that the resistance R and the capacitance C of the capacitor are related by

$$RC = \frac{\kappa \epsilon_0}{\sigma}$$

(b) Find the resistance between the plates of a 14.0-nF capacitor with a fused quartz dielectric.

45. Review. A parallel-plate capacitor consists of square plates of edge length ℓ that are separated by a distance d , where $d \ll \ell$. A potential difference ΔV is maintained between the plates. A material of dielectric constant κ fills half the space between the plates. The dielectric slab is withdrawn from the capacitor as shown in Figure P26.45. (a) Find the capacitance when the left edge of the dielectric is at a distance x from the center of the capacitor. (b) If the dielectric is removed at a constant speed v , what is the current in the circuit as the dielectric is being withdrawn?

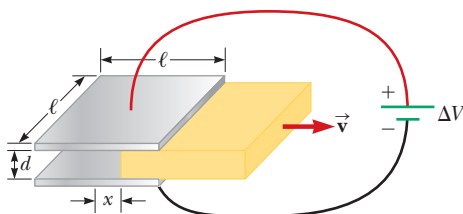


Figure P26.45

46. The current–voltage characteristic curve for a semiconductor diode as a function of temperature T is given by

$$I = I_0 (e^{e\Delta V/k_B T} - 1)$$

Here the first symbol e represents Euler's number, the base of natural logarithms. The second e is the magnitude of the electron charge, the k_B stands for Boltzmann's constant, and T is the absolute temperature. (a) Set up a spreadsheet to calculate I and $R = \Delta V/I$ for $\Delta V = 0.400$ V to 0.600 V in increments of 0.005 V. Assume $I_0 = 1.00$ nA. (b) Plot R versus ΔV for $T = 280$ K, 300 K, and 320 K.

47. Why is the following situation impossible? An inquisitive physics student takes a 100-W incandescent lightbulb out of its socket and measures its resistance with an ohmmeter. He measures a value of 10.5 Ω . He is able to connect an ammeter to the lightbulb socket to correctly measure the current drawn by the bulb while operating. Inserting the bulb back into the socket and operating the bulb from a 120-V source, he measures the current to be 11.4 A.

CHALLENGE PROBLEMS

48. A more general definition of the temperature coefficient of resistivity is

$$\alpha = \frac{1}{\rho} \frac{d\rho}{dT}$$

where ρ is the resistivity at temperature T . (a) Assuming α is constant, show that

$$\rho = \rho_0 e^{\alpha(T - T_0)}$$

where ρ_0 is the resistivity at temperature T_0 . (b) Using the series expansion $e^x \approx 1 + x$ for $x \ll 1$, show that the resistivity is given approximately by the expression

$$\rho = \rho_0 [1 + \alpha(T - T_0)] \quad \text{for } \alpha(T - T_0) \ll 1$$

49. A spherical shell with inner radius r_a and outer radius r_b is formed from a material of resistivity ρ . It carries current radially, with uniform density in all directions. Show that its resistance is

$$R = \frac{\rho}{4\pi} \left(\frac{1}{r_a} - \frac{1}{r_b} \right)$$

50. Material with uniform resistivity ρ is formed into a wedge as shown in Figure P26.50. Show that the resistance between face A and face B of this wedge is

$$R = \rho \frac{L}{w(y_2 - y_1)} \ln \frac{y_2}{y_1}$$

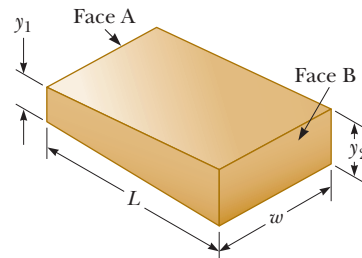


Figure P26.50

SECTION 27.4 RC Circuits

23. An uncharged capacitor and a resistor are connected in series to a source of emf. If $\mathcal{E} = 9.00 \text{ V}$, $C = 20.0 \mu\text{F}$, and $R = 100 \Omega$, find (a) the time constant of the circuit, (b) the maximum charge on the capacitor, and (c) the charge on the capacitor at a time equal to one time constant after the battery is connected.

24. Show that the time constant in Equation 27.20 has units of time.

25. In the circuit of Figure P27.25, the switch S has been open for a long time. It is then suddenly closed. Take $\mathcal{E} = 10.0 \text{ V}$, $R_1 = 50.0 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, and $C = 10.0 \mu\text{F}$. Determine the time constant (a) before the switch is closed and (b) after the switch is closed. (c) Let the switch be closed at $t = 0$. Determine the current in the switch as a function of time.

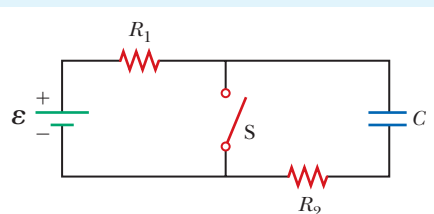


Figure P27.25 Problems 25 and 26.

26. In the circuit of Figure P27.25, the switch S has been open for a long time. It is then suddenly closed. Determine the time constant (a) before the switch is closed and (b) after the switch is closed. (c) Let the switch be closed at $t = 0$. Determine the current in the switch as a function of time.

27. A $10.0\text{-}\mu\text{F}$ capacitor is charged by a 10.0-V battery through a resistance R . The capacitor reaches a potential difference of 4.00 V in a time interval of 3.00 s after charging begins. Find R .

28. Show that the integral $\int_0^\infty e^{-2t/RC} dt$ in Example 27.11 has the value $\frac{1}{2}RC$.

SECTION 27.5 Household Wiring and Electrical Safety

29. You and your roommates are studying hard for your physics exam. You study late into the night and then fall into your bed for some sleep. You all wake early before the exam and scramble groggily around making breakfast. You can't agree on what to have, so one of you cooks waffles on a 990-watt waffle iron while another toasts bread in a 900-watt toaster. You want to make coffee with a 650-watt coffeemaker, and you plug it into the same power strip into which the waffle iron and toaster are plugged. Will the 20-A circuit breaker remain operational?

30. An electric heater is rated at $1.50 \times 10^3 \text{ W}$, a toaster at 750 W , and an electric grill at $1.00 \times 10^3 \text{ W}$. The three appliances are connected to a common 120-V household circuit. (a) How much current does each draw? (b) If the circuit is protected with a 25.0-A circuit breaker, will the circuit breaker be tripped in this situation? Explain your answer.

31. Turn on your desk lamp. Pick up the cord, with your thumb and index finger spanning the width of the cord. (a) Compute an order-of-magnitude estimate for the current in your hand. Assume the conductor inside the lamp cord next to your thumb is at potential $\sim 10^2 \text{ V}$ at a typical instant and the conductor next to your index finger is at ground potential (0 V). The resistance of your hand depends strongly on

the thickness and the moisture content of the outer layers of your skin. Assume the resistance of your hand between fingertip and thumb tip is $\sim 10^4 \Omega$. You may model the cord as having rubber insulation. State the other quantities you measure or estimate and their values. Explain your reasoning. (b) Suppose your body is isolated from any other charges or currents. In order-of-magnitude terms, estimate the potential difference between your thumb where it contacts the cord and your finger where it touches the cord.

ADDITIONAL PROBLEMS

32. Four resistors are connected in parallel across a 9.20-V battery. They carry currents of 150 mA , 45.0 mA , 14.0 mA , and 4.00 mA . If the resistor with the largest resistance is replaced with one having twice the resistance, (a) what is the ratio of the new current in the battery to the original current? (b) **What If?** If instead the resistor with the smallest resistance is replaced with one having twice the resistance, what is the ratio of the new total current to the original current? (c) On a February night, energy leaves a house by several energy leaks, including $1.50 \times 10^3 \text{ W}$ by conduction through the ceiling, 450 W by infiltration (air-flow) around the windows, 140 W by conduction through the basement wall above the foundation sill, and 40.0 W by conduction through the plywood door to the attic. To produce the biggest saving in heating bills, which one of these energy transfers should be reduced first? Explain how you decide. Clifford Swartz suggested the idea for this problem.

33. Find the equivalent resistance between points a and b in Figure P27.33.

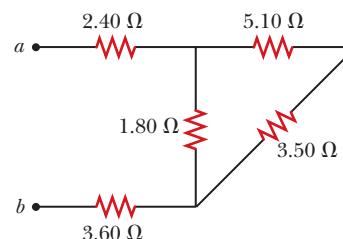


Figure P27.33

34. The circuit in Figure P27.34a consists of three resistors and one battery with no internal resistance. (a) Find the current in the $5.00\text{-}\Omega$ resistor. (b) Find the power delivered to the $5.00\text{-}\Omega$ resistor. (c) In each of the circuits in Figures P27.34b, P27.34c, and P27.34d, an additional 15.0-V battery has

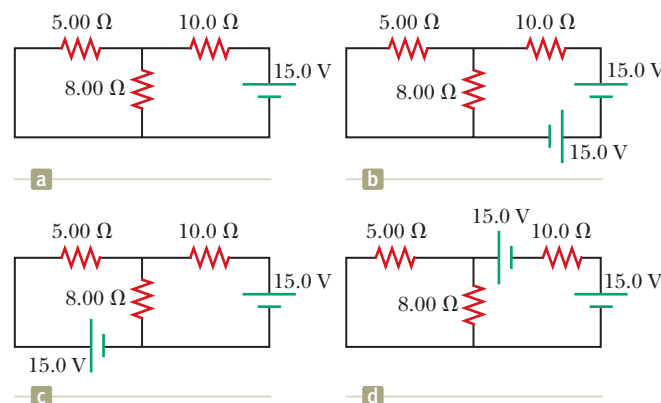


Figure P27.34

been inserted into the circuit. Which diagram or diagrams represent a circuit that requires the use of Kirchhoff's rules to find the currents? Explain why. (d) In which of these three new circuits is the smallest amount of power delivered to the $10.0\text{-}\Omega$ resistor? (You need not calculate the power in each circuit if you explain your answer.)

35. The circuit in Figure P27.35 has been connected for several seconds. Find the current (a) in the 4.00-V battery, (b) in the $3.00\text{-}\Omega$ resistor, (c) in the 8.00-V battery, and (d) in the 3.00-V battery. (e) Find the charge on the capacitor.

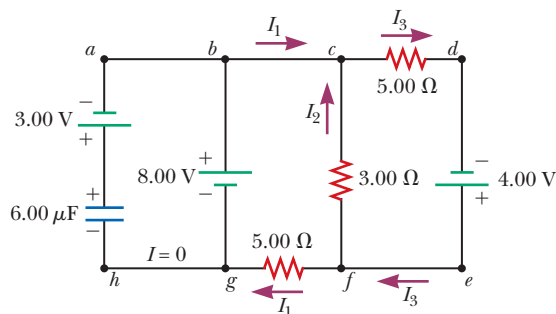


Figure P27.35

36. The resistance between terminals a and b in Figure P27.36 is $75.0\text{ }\Omega$. If the resistors labeled R have the same value, determine R .

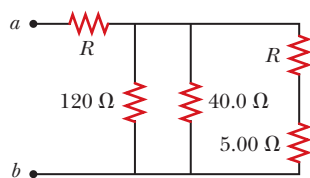


Figure P27.36

37. (a) Calculate the potential difference between points a and b in Figure P27.37 and (b) identify which point is at the higher potential.

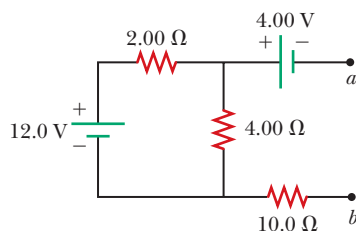


Figure P27.37

38. Why is the following situation impossible? A battery has an emf of $\mathcal{E} = 9.20\text{ V}$ and an internal resistance of $r = 1.20\text{ }\Omega$. A resistance R is connected across the battery and extracts from it a power of $P = 21.2\text{ W}$.

39. When two unknown resistors are connected in series with a battery, the battery delivers 225 W and carries a total current of 5.00 A . For the same total current, 50.0 W is delivered when the resistors are connected in parallel. Determine the value of each resistor.

40. When two unknown resistors are connected in series with a battery, the battery delivers total power P_s and carries a total current of I . For the same total current, a total power

P_p is delivered when the resistors are connected in parallel. Determine the value of each resistor.

41. The circuit in Figure P27.41 contains two resistors, $R_1 = 2.00\text{ k}\Omega$ and $R_2 = 3.00\text{ k}\Omega$, and two capacitors, $C_1 = 2.00\text{ }\mu\text{F}$ and $C_2 = 3.00\text{ }\mu\text{F}$, connected to a battery with emf $\mathcal{E} = 120\text{ V}$. If there are no charges on the capacitors before switch S is closed, determine the charges on capacitors (a) C_1 and (b) C_2 as functions of time, after the switch is closed.

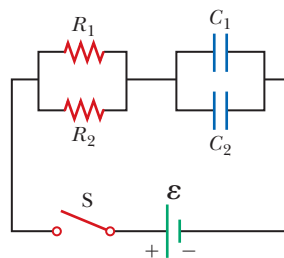


Figure P27.41

42. Two resistors R_1 and R_2 are in parallel with each other. Together they carry total current I . (a) Determine the current in each resistor. (b) Prove that this division of the total current I between the two resistors results in less power delivered to the combination than any other division. It is a general principle that *current in a direct current circuit distributes itself so that the total power delivered to the circuit is a minimum*.

43. A power supply has an open-circuit voltage of 40.0 V and an internal resistance of $2.00\text{ }\Omega$. It is used to charge two storage batteries connected in series, each having an emf of 6.00 V and internal resistance of $0.300\text{ }\Omega$. If the charging current is to be 4.00 A , (a) what additional resistance should be added in series? At what rate does the internal energy increase in (b) the supply, (c) in the batteries, and (d) in the added series resistance? (e) At what rate does the chemical energy increase in the batteries?

44. A battery is used to charge a capacitor through a resistor as shown in Figure P27.44. Show that half the energy supplied by the battery appears as internal energy in the resistor and half is stored in the capacitor.

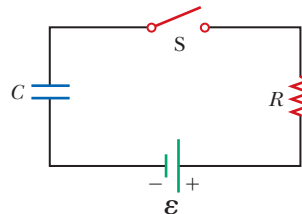


Figure P27.44

45. An ideal voltmeter connected across a certain fresh 9-V battery reads 9.30 V , and an ideal ammeter briefly connected across the same battery reads 3.70 A . We say the battery has an open-circuit voltage of 9.30 V and a short-circuit current of 3.70 A . Model the battery as a source of emf \mathcal{E} in series with an internal resistance r as in Figure 27.1a. Determine both (a) \mathcal{E} and (b) r . An experimenter connects two of these identical batteries together as shown in Figure P27.45. Find (c) the open-circuit

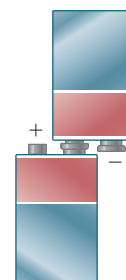


Figure P27.45

voltage and (d) the short-circuit current of the pair of connected batteries. (e) The experimenter connects a $12.0\text{-}\Omega$ resistor between the exposed terminals of the connected batteries. Find the current in the resistor. (f) Find the power delivered to the resistor. (g) The experimenter connects a second identical resistor in parallel with the first. Find the power delivered to each resistor. (h) Because the same pair of batteries is connected across both resistors as was connected across the single resistor, why is the power in part (g) not the same as that in part (f)?

- 46. Q/C** (a) Determine the equilibrium charge on the capacitor in the circuit of Figure P27.46 as a function of R . (b) Evaluate the charge when $R = 10.0\ \Omega$. (c) Can the charge on the capacitor be zero? If so, for what value of R ? (d) What is the maximum possible magnitude of the charge on the capacitor? For what value of R is it achieved? (e) Is it experimentally meaningful to take $R = \infty$? Explain your answer. If so, what charge magnitude does it imply?

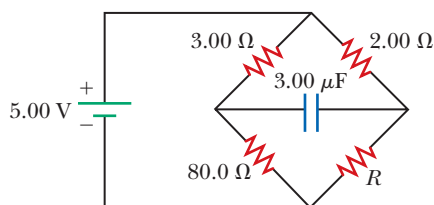


Figure P27.46

- 47.** In Figure P27.47, suppose the switch has been closed for a time interval sufficiently long for the capacitor to become fully charged. Find (a) the steady-state current in each resistor and (b) the charge Q_{max} on the capacitor. (c) The switch is now opened at $t = 0$. Write an equation for the current in R_2 as a function of time and (d) find the time interval required for the charge on the capacitor to fall to one-fifth its initial value.

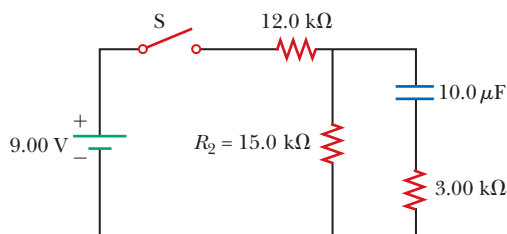


Figure P27.47

- 48. S** Figure P27.48 shows a circuit model for the transmission of an electrical signal such as cable TV to a large number of subscribers. Each subscriber connects a load resistance R_L between the transmission line and the ground. The ground is assumed to be at zero potential and able to carry any current between any ground connections with negligible resistance. The resistance of the transmission line between the connection points of different subscribers is modeled as the constant resistance R_T . Show that the equivalent resistance across the signal source is

$$R_{\text{eq}} = \frac{1}{2} [(4R_T R_L + R_T^2)^{1/2} + R_T]$$

Suggestion: Because the number of subscribers is large, the equivalent resistance would not change noticeably if the first subscriber canceled the service. Consequently, the equivalent resistance of the section of the circuit to the right of the first load resistor is nearly equal to R_{eq} .

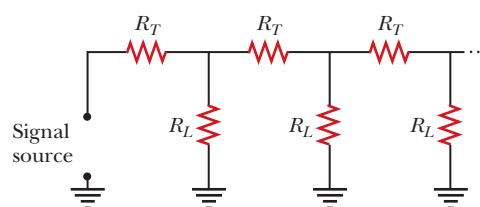


Figure P27.48

- 49.** The student engineer of a campus radio station wishes to verify the effectiveness of the lightning rod on the antenna mast (Fig. P27.49). The unknown resistance R_x is between points C and E . Point E is a true ground, but it is inaccessible for direct measurement because this

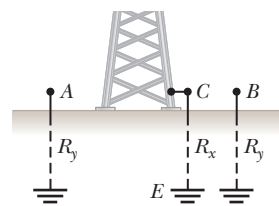


Figure P27.49

stratum is several meters below the Earth's surface. Two identical rods are driven into the ground at A and B , introducing an unknown resistance R_y . The procedure is as follows. Measure resistance R_1 between points A and B , then connect A and B with a heavy conducting wire and measure resistance R_2 between points A and C . (a) Derive an equation for R_x in terms of the observable resistances, R_1 and R_2 . (b) A satisfactory ground resistance would be $R_x < 2.00\ \Omega$. Is the grounding of the station adequate if measurements give $R_1 = 13.0\ \Omega$ and $R_2 = 6.00\ \Omega$? Explain.

- 50. S** A voltage ΔV is applied to a series configuration of n resistors, each of resistance R . The circuit components are reconnected in a parallel configuration, and voltage ΔV is again applied. Show that the power delivered to the series configuration is $1/n^2$ times the power delivered to the parallel configuration.

CHALLENGE PROBLEM

- 51. S** The switch in Figure P27.51a closes when $\Delta V_c > \frac{2}{3} \Delta V$ and opens when $\Delta V_c < \frac{1}{3} \Delta V$. The ideal voltmeter reads a potential difference as plotted in Figure P27.51b. What is the period T of the waveform in terms of R_1 , R_2 , and C ?

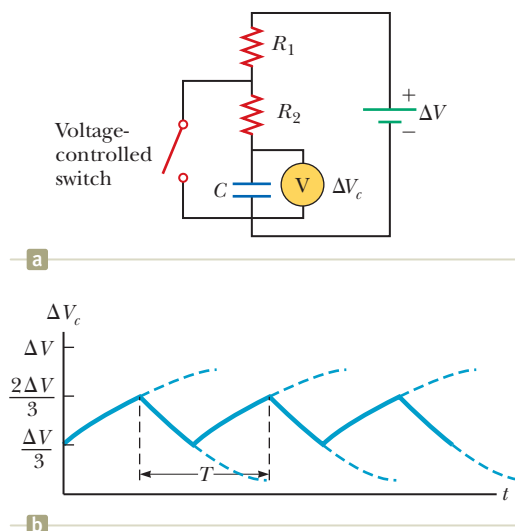


Figure P27.51